

Lecture 5: Quantum Logic

Dr Iain Styles: I.B.Styles@cs.bham.ac.uk

Last lecture, we:

- discussed various properties of qubit states

In this lecture we will:

- Introduce some common quantum logic gates
- Describe some simple quantum circuits
- Analyse simple circuits

Lecture 5: Quantum Logic – p.1/17

Lecture 5: Quantum Logic – p.1/17

Basic Quantum Logic

- We all know that modern computers are built from networks of logic gates
- Quantum computing uses logic gates in a similar way: networks of them are constructed to perform certain operations
- There are many more possible quantum gates (infinitely many)
- They must all be reversible (due to unitarity)
- So we can represent them with a unitary matrix

• Example: Quantum NOT gate: $\begin{pmatrix} a_0 \\ a_1 \end{pmatrix} \mapsto \begin{pmatrix} a_1 \\ a_0 \end{pmatrix}$

• The matrix which does this transformation is $X = \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix}$:

$$\begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix} \begin{pmatrix} a_0 \\ a_1 \end{pmatrix} = \begin{pmatrix} a_1 \\ a_0 \end{pmatrix}$$

Lecture 5: Quantum Logic – p.3/17

Lecture 5: Quantum Logic – p.3/17

Quantum Logic Gates

- The quantum analogue of the NOT gate is easy to picture
- The other classical gates that we know and “love” are not so easy to transfer to the quantum world
- All quantum gates must be reversible: classical AND, OR etc are not!
- We will not use these familiar gates as they require effort to be useful, and do not do all that we require
- We will introduce some new gates!

Controlled NOT (CNOT)

Quantum CNOT gate:

A	B	A'	B'
0	0	0	0
0	1	0	1
1	0	1	1
1	1	1	0

The transformation is therefore

$$\begin{pmatrix} a_{00} \\ a_{01} \\ a_{10} \\ a_{11} \end{pmatrix} \mapsto \begin{pmatrix} a_{00} \\ a_{01} \\ a_{11} \\ a_{10} \end{pmatrix}$$

and is represented by the matrix $N_C =$

$$N_C = \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix}$$

Controlled-Controlled NOT

Quantum CCN Gate:

A	B	C	A'	B'	C'
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	1
1	1	1	1	1	0

$$\begin{pmatrix} a_{000} \\ a_{001} \\ a_{010} \\ a_{011} \\ a_{100} \\ a_{101} \\ a_{110} \\ a_{111} \end{pmatrix} \mapsto \begin{pmatrix} a_{000} \\ a_{001} \\ a_{010} \\ a_{011} \\ a_{100} \\ a_{101} \\ a_{111} \\ a_{110} \end{pmatrix} \text{ with matrix } N_{CC} = \begin{pmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \end{pmatrix}$$

Controlled Exchange

Quantum CEX Gate:

A	B	C	A'	B'	C'
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	0	1
1	1	1	1	1	1

$$\begin{pmatrix} a_{000} \\ a_{001} \\ a_{010} \\ a_{011} \\ a_{100} \\ a_{101} \\ a_{110} \\ a_{111} \end{pmatrix} \mapsto \begin{pmatrix} a_{000} \\ a_{001} \\ a_{010} \\ a_{011} \\ a_{100} \\ a_{101} \\ a_{111} \\ a_{110} \end{pmatrix} \text{ with matrix } X_C = \begin{pmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{pmatrix}$$

Quantum Gates with no Classical Counterpart

- The NOT, CN, CCN and CEX gates are all gates which can exist in both classical and quantum worlds
- There are many other gates with no classical analogue:

- The Y and Z gates: $Y = \begin{pmatrix} 0 & -i \\ i & 0 \end{pmatrix}$, $Z = \begin{pmatrix} 1 & 0 \\ 0 & -1 \end{pmatrix}$
- Together with the X, these are known as the *Pauli matrices*

- The Hadamard Gate: $H = \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 1 \\ 1 & -1 \end{pmatrix}$
- H is one of the most useful quantum gates: it takes classical states $(|0\rangle, |1\rangle)$ to states “halfway” between $|0\rangle$ and $|1\rangle$:

$$H|0\rangle = \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle)$$


$$H|1\rangle = \frac{1}{\sqrt{2}}(|0\rangle - |1\rangle)$$

More New Gates


- We also have the Phase Gate: $S = \begin{pmatrix} 1 & 0 \\ 0 & i \end{pmatrix}$
- The T gate: $T = \begin{pmatrix} 1 & 0 \\ 0 & e^{i\frac{\pi}{4}} \end{pmatrix}$
- and the R_k gate: $R_k = \begin{pmatrix} 1 & 0 \\ 0 & e^{2\pi i/2^k} \end{pmatrix}$
- Note that $S = R_2$ and $T = R_3$
- These seem a bit arbitrary, but all have been found to be useful in various quantum algorithms. We'll be using some of them later.

Analysing Quantum Circuits

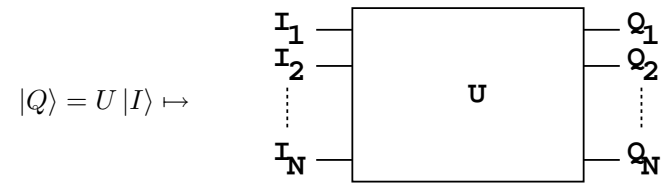- So far, we've represented quantum gates with matrices
- It will often be useful to adopt a graphical representation:



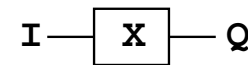
- Each I/O line represents one qubit, e.g, for the X gate:



- The analysis of circuits made from quantum gates is quite straightforward: all we have to do is apply the matrices in the right order

A Simple Circuit


Example: NOT-NOT

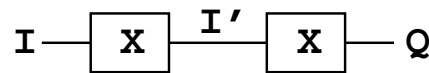


- Let $|I\rangle = \begin{pmatrix} a_0 \\ a_1 \end{pmatrix}$. Then $|I'\rangle = X |I\rangle = \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix} \begin{pmatrix} a_0 \\ a_1 \end{pmatrix} = \begin{pmatrix} a_1 \\ a_0 \end{pmatrix}$
- We then have $|Q\rangle = X |I'\rangle = \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix} \begin{pmatrix} a_1 \\ a_0 \end{pmatrix} = \begin{pmatrix} a_0 \\ a_1 \end{pmatrix}$
- This is what we would expect from NOT-NOT: no change
- We write this as $|Q\rangle = X |I'\rangle = X X |I\rangle = X^2 |I\rangle$
- Note that $X^2 = \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix} \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix} = \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix}$, and we can express the entire circuit with a single matrix!

Another Example

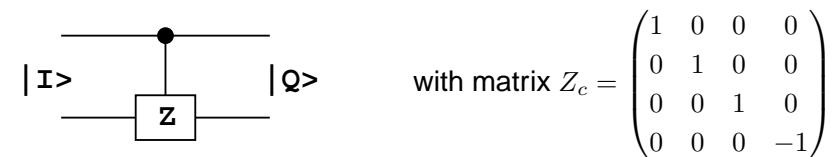In this example, we will use the Controlled-Z gate:



Consider the circuit

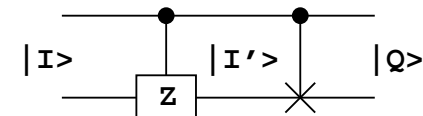

It should be clear that $|I'\rangle = Z_c |I\rangle$, and $|Q\rangle = N_c |I'\rangle$.


So $|Q\rangle = N_c Z_c |I\rangle$ (note the order)

Then $N_c Z_c = \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix} \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 \end{pmatrix} = \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & -1 \\ 0 & 0 & 1 & 0 \end{pmatrix}$

A Harder Example

- In the algorithms we will study next week, we will need to be able to analyse circuits which contain both one- and two-input gate. This is a bit more complicated.

- Consider the circuit

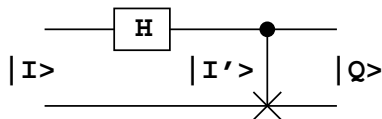

- Clearly $|Q\rangle = N_c |I'\rangle$, but how do we find matrix M such that $|I'\rangle = M |I\rangle$?
- The Hadamard gate H only acts on one bit of our state
- Its action on the first bit is $H |0\rangle = \frac{1}{\sqrt{2}} (|0\rangle + |1\rangle)$, and $H |1\rangle = \frac{1}{\sqrt{2}} (|0\rangle - |1\rangle)$
- $|I\rangle$ is defined on the basis $\{|00\rangle, |01\rangle, |10\rangle, |11\rangle\}$

A Harder Example

- So $|I'\rangle = M |I\rangle$ and hence $|Q\rangle = M |I'\rangle = N_c M |I\rangle$. We need to calculate

$$N_c M = \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix} \begin{pmatrix} 1 & 0 & 1 & 0 \\ 0 & 1 & 0 & 1 \\ 1 & 0 & -1 & 0 \\ 0 & 1 & 0 & -1 \end{pmatrix} = \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 0 & 1 & 0 \\ 0 & 1 & 0 & 1 \\ 0 & 1 & 0 & -1 \\ 1 & 0 & -1 & 0 \end{pmatrix}$$

- This is unitary, as required and expected
- This is actually quite an important quantum circuit: it acts on the basis states in the following way:

$$\begin{aligned} |00\rangle &\mapsto \frac{1}{\sqrt{2}} (|00\rangle + |11\rangle) & |01\rangle &\mapsto \frac{1}{\sqrt{2}} (|01\rangle + |10\rangle) \\ |10\rangle &\mapsto \frac{1}{\sqrt{2}} (|00\rangle - |11\rangle) & |11\rangle &\mapsto \frac{1}{\sqrt{2}} (|01\rangle - |10\rangle) \end{aligned}$$

A Harder Example


- The basis states transform in the following way:

$$\begin{aligned} |00\rangle &\mapsto \frac{1}{\sqrt{2}} (|00\rangle + |10\rangle) \\ |01\rangle &\mapsto \frac{1}{\sqrt{2}} (|01\rangle + |11\rangle) \\ |10\rangle &\mapsto \frac{1}{\sqrt{2}} (|00\rangle - |10\rangle) \\ |11\rangle &\mapsto \frac{1}{\sqrt{2}} (|01\rangle - |11\rangle) \end{aligned}$$

- The matrix for this is $M = \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 0 & 1 & 0 \\ 0 & 1 & 0 & 1 \\ 1 & 0 & -1 & 0 \\ 0 & 1 & 0 & -1 \end{pmatrix}$

Creating Bell States

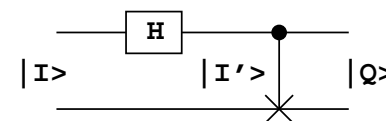- The new states are all entangled pairs (Bell states): if one of the qubits is measured, we automatically know what the other one is without measuring it
- Starting with an initially independent set of qubits, we can form a composite state and pass it through this circuit in order to create entangled pairs



Conclusions

this lecture we have:

- Introduced some common quantum logic gates
- Shown how to analyse networks of quantum logic gates
- Shown how to create entangled pairs using quantum logic gates

next lecture we will:

- Introduce the Quantum Fourier Transform